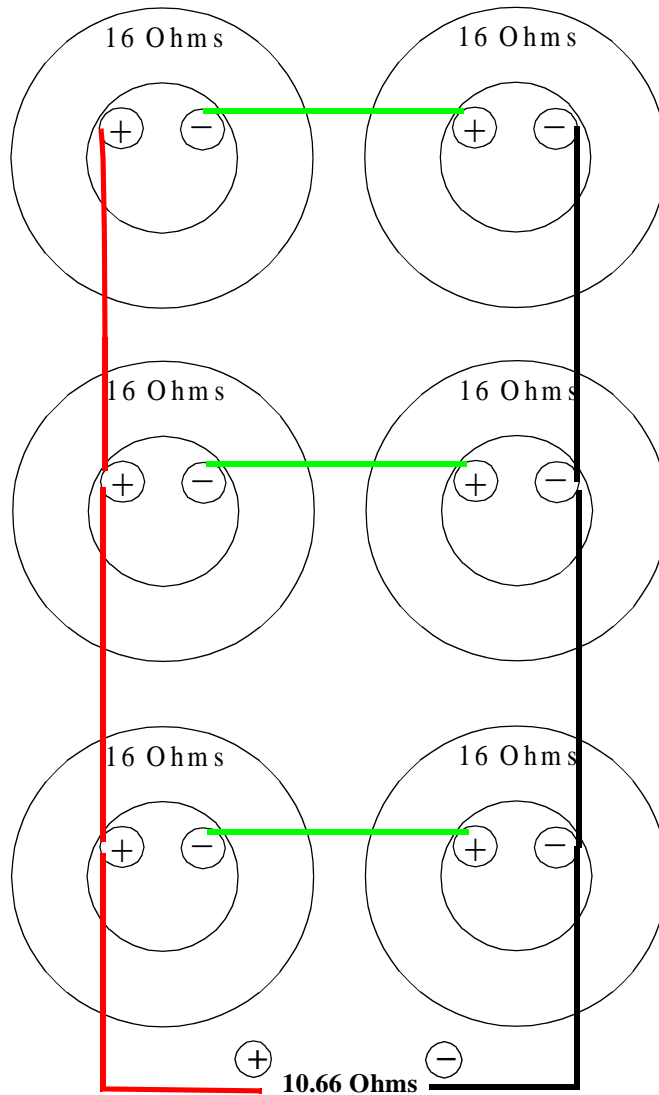


6x10 Cab (Sound City L610) Wiring Diagram




Six 16-Ohm speakers
wired in parallel-series to
yield a total load of 10.66 Ohms.

Formulae:

$$1/(1/(16+16) + 1/(16 + 16) + 1/(16 + 16))$$

$$1/(1/32 + 1/32 + 1/32) = 10.66$$

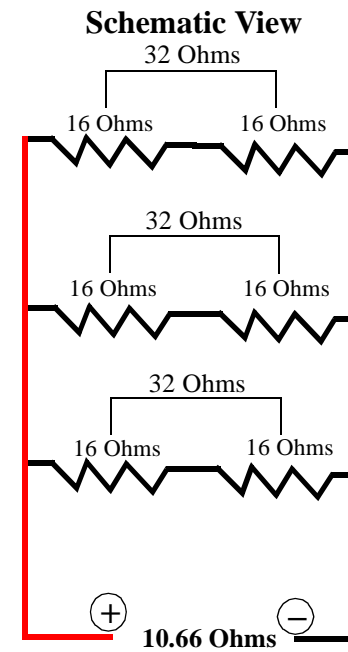

Remember that 10.66 is Re, so
set your amp's OT tap for 16 ohms.