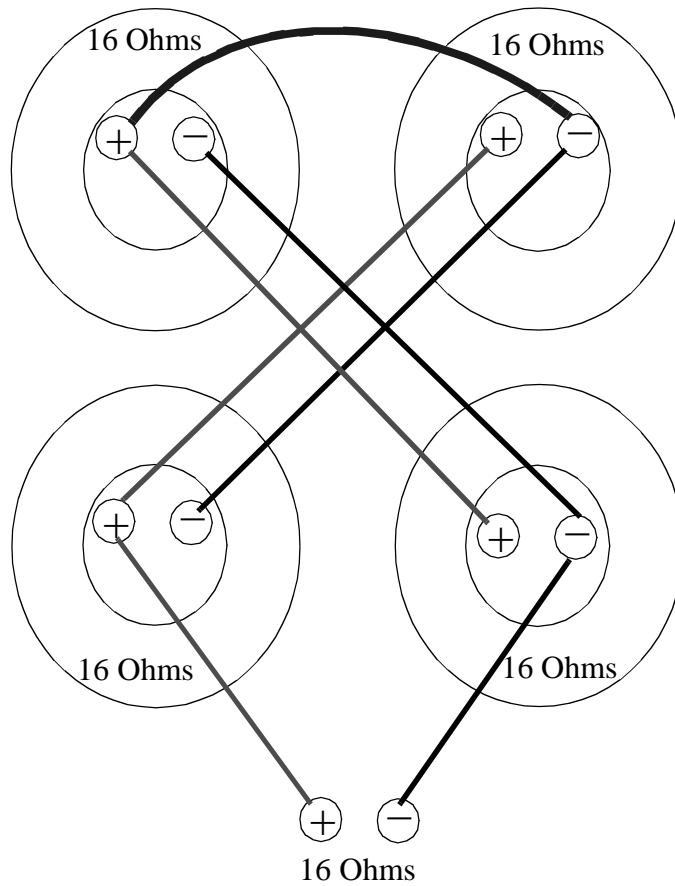


Series-Parallel X-Pattern Wiring Diagram for two Different Pairs of Speakers

Series-Parallel X-Pattern Wiring



Use this wiring scheme if you have two different pairs of speakers and want to wire them in an X-pattern.

Four 16-Ohm speakers wired in series-parallel to yield a total load of 16 Ohms.
 Formula:
 $1/(1/16+1/16) + 1(1/16+1/16) = 16$
 where... $1/(1/16+1/16) = 8$
 Ⓢ = combined parallel load

Schematic View

